

Homework 2

RTL Design of a Randomizer

1 Purpose

- This HW is a pre-requisite for Lab2 which will be covered in another document
- The objectives of this homework are:
 - RTL implementation of a randomizer
 - Validation of the design using self-checking testbenches and simulation

2 Required tools

Notepad++ (source code editing)

ModelSim PE student editions (simulation)

3 Part A: PRBS Generator

- Using a linear feedback shift register (LFSR), design a pseudo random binary sequence (PRBS) generator that implements the polynomial $1 + X^{14} + X^{15}$ shown in Figure 1 which is used to randomize a sequence of binary inputs.
- The randomizer is initialized with the vector:
 - [LSB] 0 1 1 0 1 1 1 0 0 0 1 0 1 0 1 [MSB].
- In addition to clock (`clk`) and asynchronous reset (`reset`), include a synchronous seed load (`load`) and clock enable (`en`) inputs
- Validation: using the following input data sequence and the corresponding data output to validate your design
 - Input Data (Hex):
 - AC BC D2 11 4D AE 15 77 C6 DB F4 C9
 - Randomized Data (Hex):
 - 55 8A C4 A5 3A 17 24 E1 63 AC 2B F9

 


Figure 1: PRBS generator for Data randomization

Table 1: Intermediate data values for validation

Initialized vector 011 0111 0001 0101

No	Shift Register															XOR #1	Data in		Data out	
	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15		0x	0b	0b	0x
1	0	1	1	0	1	1	1	0	0	0	1	0	1	0	1	1	A	1	0	5
2	1	0	1	1	0	1	1	1	0	0	0	1	0	1	0	1		0	1	
3	1	1	0	1	1	0	1	1	1	0	0	0	1	0	1	1		1	0	
4	1	1	1	0	1	1	0	1	1	1	0	0	0	1	0	1		0	1	
5	1	1	1	1	0	1	1	0	1	1	1	0	0	0	1	1	C	1	0	5
6	1	1	1	1	1	0	1	1	0	1	1	1	0	0	0	0		1	1	
7	0	1	1	1	1	1	0	1	1	0	1	1	1	0	0	0		0	0	
8	0	0	1	1	1	1	1	0	1	1	0	1	1	1	0	1		0	1	
9	1	0	0	1	1	1	1	1	0	1	1	0	1	1	1	0	B	1	1	8
10	0	1	0	0	1	1	1	1	1	0	1	1	0	1	1	0		0	0	
11	0	0	1	0	0	1	1	1	1	1	0	1	1	0	1	1		1	0	
12	1	0	0	1	0	0	1	1	1	1	1	0	1	1	0	1		1	0	
13	1	1	0	0	1	0	0	1	1	1	1	1	0	1	1	0	C	1	1	A
14	0	1	1	0	0	1	0	0	1	1	1	1	1	0	1	1		1	0	
15	1	0	1	1	0	0	1	0	0	1	1	1	1	1	0	1		0	1	
16	1	1	0	1	1	0	0	1	0	0	1	1	1	1	1	0		0	0	
17	0	1	1	0	1	1	0	0	1	0	0	1	1	1	1	0	D	1	1	C
18	0	0	1	1	0	1	1	0	0	1	0	0	1	1	1	0		1	1	
19	0	0	0	1	1	0	1	1	0	0	1	0	0	1	1	0		0	0	
20	0	0	0	0	1	1	0	1	1	0	0	1	0	0	1	1		1	0	
21	1	0	0	0	0	1	1	0	1	1	0	0	1	0	0	0	2	0	0	4
22	0	1	0	0	0	0	1	1	0	1	1	0	0	1	0	1		0	1	
23	1	0	1	0	0	0	0	1	1	0	1	1	0	0	1	1		1	0	
24	1	1	0	1	0	0	0	0	1	1	0	1	1	0	0	0		0	0	
25	0	1	1	0	1	0	0	0	0	1	1	0	1	1	0	1	1	0	1	A
26	1	0	1	1	0	1	0	0	0	0	1	1	0	1	1	0		0	0	
27	0	1	0	1	1	0	1	0	0	0	0	1	1	0	1	1		0	1	
28	1	0	1	0	1	1	0	1	0	0	0	0	1	1	0	1		1	0	
29	1	1	0	1	0	1	1	0	1	0	0	0	0	1	1	0	1	0	0	5
30	0	1	1	0	1	0	1	1	0	1	0	0	0	0	1	1		0	1	
31	1	0	1	1	0	1	0	1	1	0	1	0	0	0	0	0		0	0	
32	0	1	0	1	1	0	1	0	1	1	0	1	0	0	0	0		1	1	
33	0	0	1	0	1	1	0	1	0	1	1	0	1	0	0	0	4	0	0	3
34	0	0	0	1	0	1	1	0	1	0	1	1	0	1	0	1		1	0	
35	1	0	0	0	1	0	1	1	0	1	0	1	1	0	1	1		0	1	
36	1	1	0	0	0	1	0	1	1	0	1	0	1	1	0	1		0	1	
37	1	1	1	0	0	0	1	0	1	1	0	1	0	1	1	0	D	1	1	A
38	0	1	1	1	0	0	0	1	0	1	1	0	1	0	1	1		1	0	
39	1	0	1	1	1	0	0	0	1	0	1	1	0	1	0	1		0	1	
40	1	1	0	1	1	1	0	0	0	1	0	1	1	0	1	1		1	0	
41	1	1	1	0	1	1	1	0	0	0	1	0	1	1	0	1	A	1	0	1

42	1	1	1	1	0	1	1	1	0	0	0	1	0	1	1	0		0	0	
43	0	1	1	1	1	0	1	1	1	0	0	0	1	0	1	1		1	0	
44	1	0	1	1	1	1	0	1	1	1	0	0	0	1	0	1		0	1	
45	1	1	0	1	1	1	1	0	1	1	1	0	0	0	1	1		1	0	
46	1	1	1	0	1	1	1	1	0	1	1	1	0	0	0	0	E	1	1	7
47	0	1	1	1	0	1	1	1	1	0	1	1	1	0	0	0		1	1	
48	0	0	1	1	1	0	1	1	1	1	0	1	1	1	0	1		0	1	
49	1	0	0	1	1	1	0	1	1	1	1	0	1	1	1	0		0	0	
50	0	1	0	0	1	1	1	0	1	1	1	1	0	1	1	0	1	0	0	2
51	0	0	1	0	0	1	1	1	0	1	1	1	1	0	1	1	1	0	1	
52	1	0	0	1	0	0	1	1	1	0	1	1	1	1	1	0	1	1	0	
53	1	1	0	0	1	0	0	1	1	1	0	1	1	1	1	1		0	0	
54	0	1	1	0	0	1	0	0	1	1	1	0	1	1	1	1		0	1	4
55	0	0	1	1	0	0	1	0	0	1	1	1	0	1	1	1	5	0	0	
56	0	0	0	1	1	0	0	1	0	0	1	1	1	0	1	1		1	0	
57	1	0	0	0	1	1	0	0	1	0	0	1	1	1	1	0		0	1	
58	1	1	0	0	0	1	1	0	0	1	0	0	1	1	1	1	7	1	1	E
59	0	1	1	0	0	0	1	1	0	0	1	0	0	1	1	1		1	1	
60	0	0	1	1	0	0	0	1	1	0	0	1	0	0	1	1		1	0	
61	1	0	0	1	1	0	0	0	1	1	0	0	1	0	0	0		0	0	
62	0	1	0	0	1	1	0	0	0	1	1	0	0	1	0	1	7	1	0	1
63	1	0	1	0	0	1	1	0	0	0	1	1	0	0	1	1		1	0	
64	1	1	0	1	0	0	1	1	0	0	0	1	1	0	0	0		1	1	
65	0	1	1	0	1	0	0	1	1	0	0	0	1	1	1	0		1	0	
66	1	0	1	1	0	1	0	0	1	1	0	0	0	1	1	1	C	1	1	6
67	0	1	0	1	1	0	1	0	0	1	1	0	0	0	1	1		0	1	
68	1	0	1	0	1	1	0	1	0	0	1	1	0	0	0	0		0	0	
69	0	1	0	1	0	1	1	0	1	0	0	1	1	0	0	0		0	0	
70	0	0	1	0	1	0	1	1	0	1	0	0	1	1	1	0	6	1	0	3
71	1	0	0	1	0	1	0	1	1	0	1	0	0	1	1	1		1	1	
72	0	1	0	0	1	0	1	0	1	1	0	1	0	0	1	1		0	1	
73	1	0	1	0	0	1	0	1	0	1	1	0	1	0	0	0		0	1	
74	0	1	0	1	0	0	1	0	1	0	1	1	0	1	0	1	D	1	0	A
75	1	0	1	0	1	0	0	1	0	1	0	1	1	0	1	1		0	1	
76	1	1	0	1	0	1	0	0	1	0	1	0	1	1	1	0		1	0	
77	1	1	1	0	1	0	1	0	0	1	0	1	0	1	1	1		0	1	
78	0	1	1	1	0	1	0	1	0	0	1	0	1	0	1	1	B	0	1	C
79	1	0	1	1	1	0	1	0	1	0	0	1	0	1	0	1		1	0	
80	1	1	0	1	1	1	0	1	0	1	0	0	1	0	1	1		1	0	
81	1	1	1	0	1	1	1	0	1	0	1	0	0	1	0	1		1	0	
82	1	1	1	1	0	1	1	1	0	1	0	1	0	0	1	1		1	0	2
83	1	1	1	1	1	0	1	1	1	0	1	0	1	0	0	0	F	1	1	
84	0	1	1	1	1	1	0	1	1	1	0	1	0	1	0	1		1	0	
85	1	0	1	1	1	1	1	0	1	1	1	0	1	0	1	1		0	1	
86	1	1	0	1	1	1	1	1	0	1	1	1	0	1	0	1	4	1	0	B
87	1	1	1	0	1	1	1	1	1	0	1	1	1	0	1	1		0	1	
88	1	1	1	1	0	1	1	1	1	1	0	1	1	1	0	1		0	1	
89	1	1	1	1	1	0	1	1	1	1	1	0	1	1	1	1	C	1	1	F

90	0	1	1	1	1	1	0	1	1	1	1	1	0	1	1	0		1	1	
91	0	0	1	1	1	1	1	0	1	1	1	1	1	0	1	1		0	1	
92	1	0	0	1	1	1	1	1	0	1	1	1	1	1	0	1		0	1	
93	1	1	0	0	1	1	1	1	1	0	1	1	1	1	1	0	9	1	1	9
94	0	1	1	0	0	1	1	1	1	1	0	1	1	1	1	0		0	0	
95	0	0	1	1	0	0	1	1	1	1	0	1	1	1	1	0		0	0	
96	0	0	0	1	1	0	0	1	1	1	1	1	0	1	1	0		1	1	

3.1 Submission

Name the RTL module as `prbs.vhd`. Create a testbench to verify the functionality of `prbs.vhd` using self-checking testbench. Name this testbench `prbs_tb.vhd`

4 Part B: PRBS verify wrapper

The PRBS verify wrapper (`prbs_verify`) is shown in Figure 2. It encloses the `prbs` module, a ROM (constant register) that holds the value of the seed (`seed_rom`), a second ROM (`in_data_rom`) that holds the test value of the input data sequence (`data_in`), a third ROM (`out_data_rom`) that holds the expected value of the output data sequence (`data_out`), and a block that contains a verifying logic to check the output data sequence against the values of the data stored in the output data ROM. If there is no mismatch, then the `pass` output is asserted. The `prbs_verify` module takes an input clock (`clk`), an active high reset, a seed load input (`load`), and an enable input (`en`). Those inputs are passed through to the `prbs` block. The input clock is connected to the 50 MHz clock on DE0-CV board. The reset input is connected to a push button switch. Both `load` and `en` are connecting to a sliding switch. The `pass` output is connected to a LED.

 


Figure 2: PRBS verify wrapper

4.1 Submission

- a. Design an RTL implementation of the PRBS verifier shown Figure 2. Name the file `prbs_verify.vhd`
- b. Design a testbench to verify the functionality of `prbs_verify`. Name this testbench `prbs_verify_tb.vhd`.
- c. Create a simulation project and simulate the three files: `prbs.vhd`, `prbs_verify.vhd`, and `prbs_verify_tb.vhd`